

SYNCHRONOUS BINARY UP COUNTER

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.STD_LOGIC_ARITH.ALL;
4  use IEEE.STD_LOGIC_UNSIGNED.ALL;
5  entity synbicount is
6  Port (rs,clk: in STD_LOGIC;
7  q: inout STD_LOGIC_VECTOR (3 downto 0));
8  end synbicount;
9  architecture Behavioral of synbicount is
10  signal div:std_logic_vector(22 downto 0);
11  signal temp:STD_LOGIC_VECTOR (3 downto 0);
12  signal clkd:std_logic;
13  begin
14  process(clk)
15  begin
16  if rising_edge(clk)then
17  div<= div+1;
18  end if; |
19  end process;
20  clkd<=div(22);
21  process(clkd)
22  begin
23  if(clkd='1' and clkd'event) then
24  if(rs='1') then temp<=(others=>'0');
25  else temp<=temp+1;
26  end if;
27  q<= temp;
28  end if;
29  end process;
30  end Behavioral;
```

