

MULTIPLEXER

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.STD_LOGIC_ARITH.ALL;
4  use IEEE.STD_LOGIC_UNSIGNED.ALL;
5  entity multiplexer is
6  Port ( d : in  STD_LOGIC_VECTOR (7 downto 0);
7        s : in  STD_LOGIC_VECTOR (2 downto 0);
8        f : out STD_LOGIC);
9  end multiplexer;
10 architecture Behavioral of multiplexer is
11 begin
12   f<= d(0) when s="000" else
13   d(1) when s="001" else
14   d(2) when s="010" else
15   d(3) when s="011" else
16   d(4) when s="100" else
17   d(5) when s="101" else
18   d(6) when s="110" else
19   d(7) when s="111";
20 end Behavioral;
```



