## **DEMULTIPLEXER**

```
library IEEE;
 1
        use IEEE.STD_LOGIC_1164.ALL;
 2
        use IEEE.STD_LOGIC_ARITH.ALL;
 3
 4
        use IEEE.STD_LOGIC_UNSIGNED.ALL;
 5
             entity demultiplexer is
port(f:in std_logic;
 6
      日
             s:in std_logic_vector(2 downto 0);
 8
 9
             y:out std_logic_vector(7 downto 0));
10
             end demultiplexer;
11
        architecture behavioral of demultiplexer is
12
13
      ⊟begin
             y(0)<=f when s="000"else'0';
14
            y(0)<=f when s="000"else'0';
y(1)<=f when s="001"else'0';
y(2)<=f when s="010"else'0';
y(3)<=f when s="011"else'0';
y(4)<=f when s="100"else'0';
y(5)<=f when s="101"else'0';
y(6)<=f when s="110"else'0';
d behavioral:
15
16
17
18
19
20
21
        end behavioral;
22
```



